



NED UNIVERSITY OF ENGINEERING & TECHNOLOGY
Department of Computer Science & Information Technology
CS-251 Logic Design & Switching Theory



ASSIGNMENT # 02

Question 1: Design a 4-to-2 Priority Encoder, create the truth table, logic equation and logic diagram for a 4-to-2 priority encoder.

Question 2: Describe the internal functionality and logical implementation of 74148 IC.

Question 3: Draw the logic diagram and truth table for the respective 7485 or 74LS85 magnitude comparator IC.

Question 4: Create a 5 bit comparator using IC 7485.